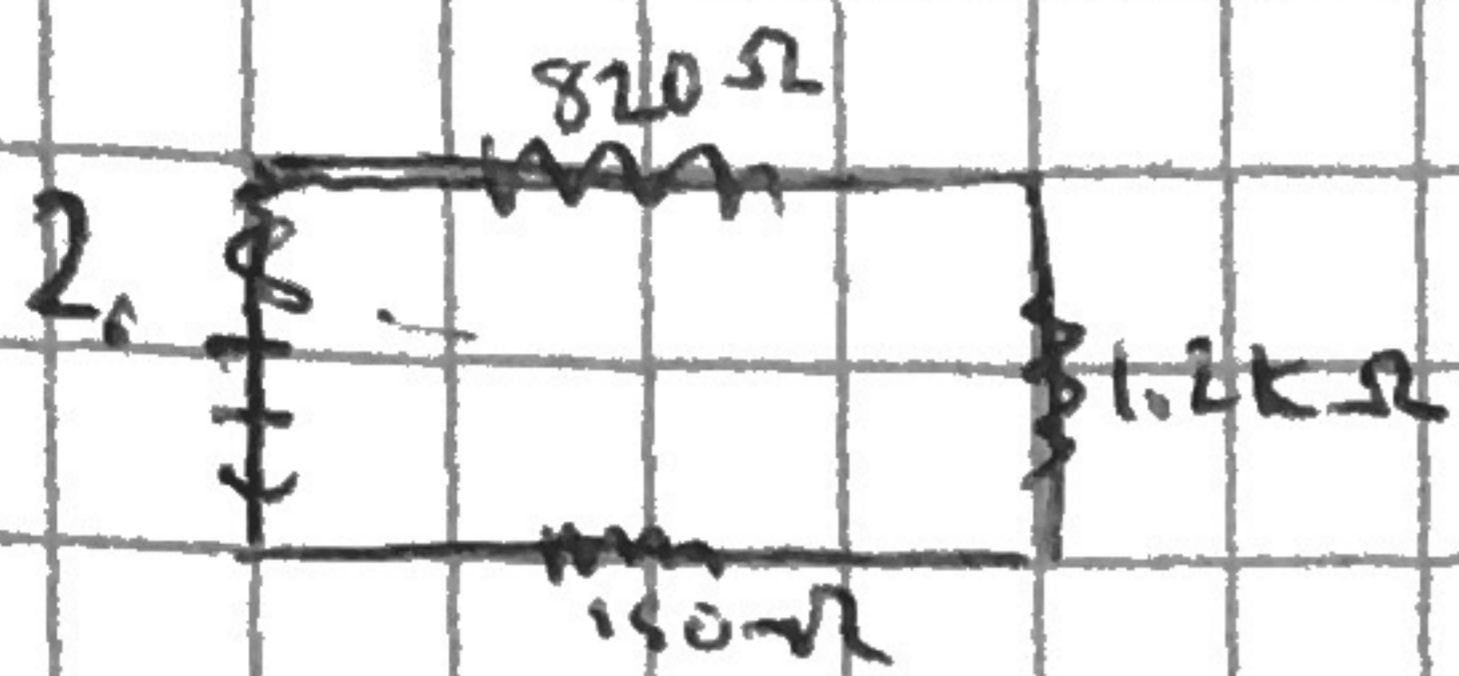


## Activity


$$1. 3.5V / 470 \Omega = 7.4 \text{ mA}$$

$$3.5V / 15.5 \mu A \cdot 0.0000035 / 0.0000155 = 226 \Omega$$


$$1.4 \text{ mA} = 22k \cdot 0.0014 \text{ A} \cdot 22,000 = 30.8V$$



$$R_T = 820 + 150 + 1200 = 2170 \Omega$$

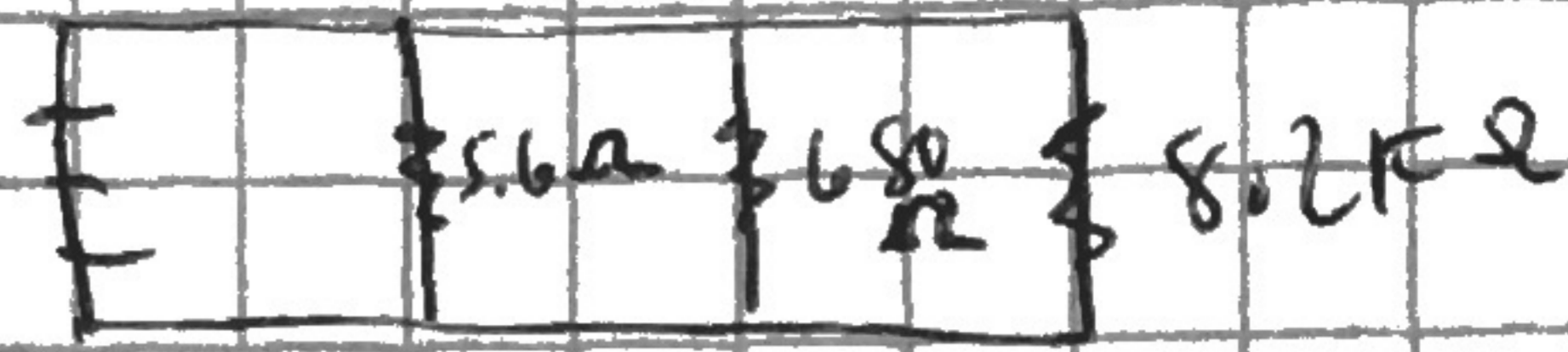
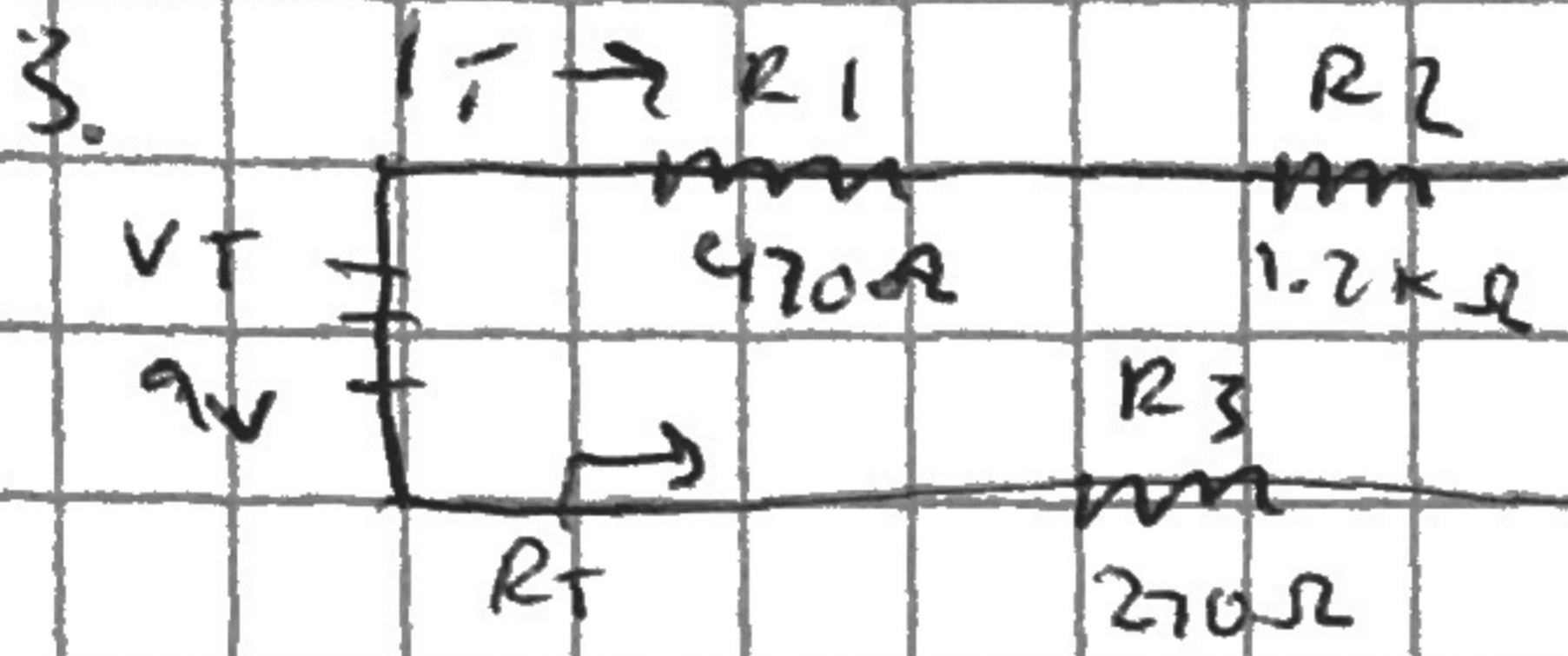
$$R_T = 5.6 + 680 + 8200 = 8885.6 \Omega$$



$$R_T = 270 + 470 + 1200$$

$$R_T = 1940 \Omega$$

$$V/R = I$$

$$9 / 1940 = 4.62 \text{ mA}$$

$$V_1 = 4.62 \text{ mA} \cdot 470$$


$$V_1 = 2.17V$$

$$V_2 = 4.62 \text{ mA} \cdot 1200$$

$$V_2 = 5.56V$$

$$V_3 = 4.62 \text{ mA} \cdot 270$$

$$V_3 = 1.25V$$

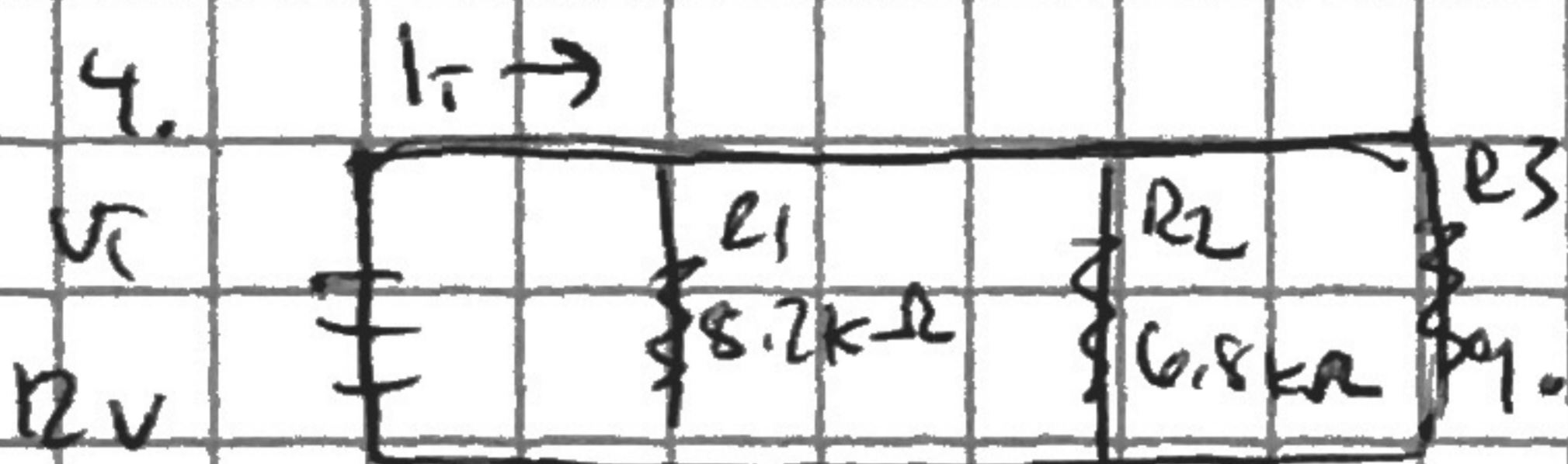

$$R_T = 8200 + 6800 + 1700$$

$$R_T = 19.7 \text{ k}\Omega$$

$$I_T = V/R \quad I = 12 / 19700$$

$$I = 0.609 \text{ mA}$$

## Conclusion

- Voltage / Resistance = Current (Series)
  - $R_T = \text{Sum of individual resistance}$
  - $V_T = \text{Sum of individual voltage drops}$

## 2. (Parallel)

- components share same voltage
- $I_T = \text{sum of individual branch currents}$

3. A series because once one resistance is taken away the voltage will not go through the rest of the wires.